

Digital Electronics

Moule-II

Ajith Kumar M M

Lecturer in electronics


MVGM, Government Polytechnic , vennikulam

Logic Circuits

- ❑ Logic circuits for digital systems may be **combinational or sequential**.
- ❑ A combinational circuit consists of **logic gates** whose outputs at any time are determined from only the **present combination of inputs**.
- ❑ A **combinational** circuit performs an operation that can **be specified logically by a set of Boolean functions**.
- ❑ Sequential circuits have **storage elements** in addition **to logic gates**.
- ❑ Their outputs are a function of the **inputs and the state of the storage elements**.
- ❑ Because the state of the storage elements is a **function of previous inputs**, the outputs of a sequential circuit depend not only on present values of inputs, but also on past inputs,

Combinational Circuits

 - ❑ A combinational circuit consists of an interconnection of logic gates.
- ❑ Combinational logic gates react to the values of the signals at their inputs and produce the value of the output signal.
- ❑ Transforming binary information from the given input data to a required output data.



Half Adder

- ❑ Half Adder circuit needs two binary inputs and two binary outputs.
- ❑ The output variables produce the sum and carry.


Half Adder

<i>x</i>	<i>y</i>	<i>C</i>	<i>S</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


Half Adder

Half Adder

<i>x</i>	<i>y</i>	<i>C</i>	<i>S</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

(a) $S = xy' + x'y$
 $C = xy$

 

(b) $S = x \oplus y$
 $C = xy$

Full Adder

- ❑ Addition of n-bit binary numbers requires the use of a full adder,
- ❑ The process of addition proceeds on a bit-by-bit basis, right to left, beginning with the least significant bit.
- ❑ After the least significant bit, addition at each position adds not only the respective bits of the words, but must also consider a possible carry bit from addition at the previous position

$$\begin{array}{r} 11 \text{ carry} \\ 0011010 = 26_{10} \\ +0001100 = 12_{10} \\ \hline 0100110 = 38_{10} \end{array}$$

Full Adder



Full Adder

<i>x</i>	<i>y</i>	<i>z</i>	<i>c</i>	<i>s</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full Adder

Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

  


$$S = \bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xyz$$

$$S = x \oplus y \oplus z$$

$$C = xy + yz + xz$$


Full Adder

 

$$S = x \oplus y \oplus z$$

$$C = xy + yz + xz$$

Half Subtractor

 

A	B	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$\text{Difference} = A \oplus B$$


$$\text{Borrow} = \bar{A}B$$

Half Subtractor


A	B	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$\text{Difference} = A \oplus B$$

$$\text{Borrow} = \bar{A}B$$

 

Full Subtractor

 

Full Subtractor

Inputs			Outputs	
A	B	Borrow _{in}	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Full Subtractor

A	BC			
	00	01	11	10
0	0	1	0	1
1	1	0	1	0

Inputs			Outputs	
A	B	Borrow _{in}	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$Diff = A\bar{B}\bar{C} + \bar{A}\bar{B}C + ABC + \bar{A}B\bar{C}$$

$$Diff = A \oplus B \oplus C$$


Full Subtractor

A \ BC				
	00	01	11	10
0		1	1	1
1			1	

Inputs			Outputs	
A	B	Borrow _{in}	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$\text{Borrow} = \bar{A}C + BC + \bar{A}B$$

Full Subtractor

 

$$Diff = A \oplus B \oplus C$$


$$Borrow = \bar{A}C + BC + \bar{A}B$$

Parallel Adder

- A single full adder performs the addition of two one-bit numbers and an input carry.
- A **Parallel Adder** is a digital circuit capable of finding the arithmetic **sum** of two binary numbers that is **greater than one bit** in length

$$\begin{array}{r} \text{Carry} \quad 1 \quad 1 \quad 1 \quad 0 \\ \quad \quad 1 \quad 0 \quad 1 \quad 1 \quad + \\ \quad \quad \underline{0 \quad 1 \quad 1 \quad 0} \\ \quad \quad 0 \quad 0 \quad 0 \quad 1 \end{array}$$

Four bit Parallel Adder

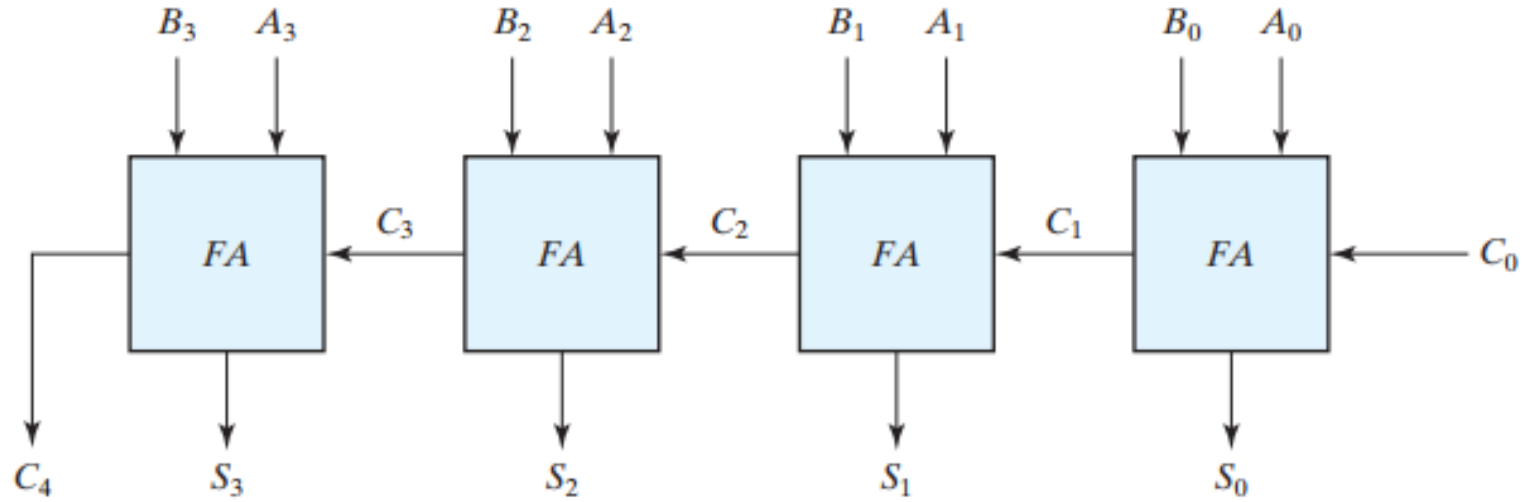

Carry 1 1 1 0


1	0	1	1		+
0	1	1	0		
<hr/>					
0	0	0	1		

Multiplexer

- ❑ **Multiplexer** is a combinational circuit that has maximum of 2^n data inputs, 'n' selection lines and single output line.
- ❑ One of these data inputs will be connected to the output based on the values of selection lines.
- ❑ Since there are 'n' selection lines, there will be 2^n possible combinations of zeros and ones. So, each combination will select only one data input.
- ❑ Multiplexer is also called as **Mux**


4x1 Multiplexer

 - ❑ 4x1 Multiplexer has four data inputs I_3 , I_2 , I_1 & I_0 , two selection lines s_1 & s_0 and one output Y .
- ❑ One of these 4 inputs will be connected to the output based on the combination of inputs present at these two selection lines.





4x1 Multiplexer

Selection Lines		Output
S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 

$$Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$


4x1 Multiplexer

  

$$Y = \bar{s}_1\bar{s}_0I_0 + \bar{s}_1s_0I_1 + s_1\bar{s}_0I_2 + s_1s_0I_3$$


De-Multiplexer

 - ❑ **De-Multiplexer** is a combinational circuit that performs the reverse operation of Multiplexer.
- ❑ It has single input, 'n' selection lines and maximum of 2^n outputs.
- ❑ The input will be connected to one of these outputs based on the values of selection line.
- ❑ De-Multiplexer is also called as **De-Mux**.




De-Multiplexer

Selection Inputs		Outputs			
S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

 

De-Multiplexer

Selection Inputs		Outputs			
S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

 

$$Y_0 = \bar{S}_1 \bar{S}_0 I$$

$$Y_1 = \bar{S}_1 S_0 I$$

$$Y_2 = S_1 \bar{S}_0 I$$

$$Y_3 = S_1 S_0 I$$

De-Multiplexer

