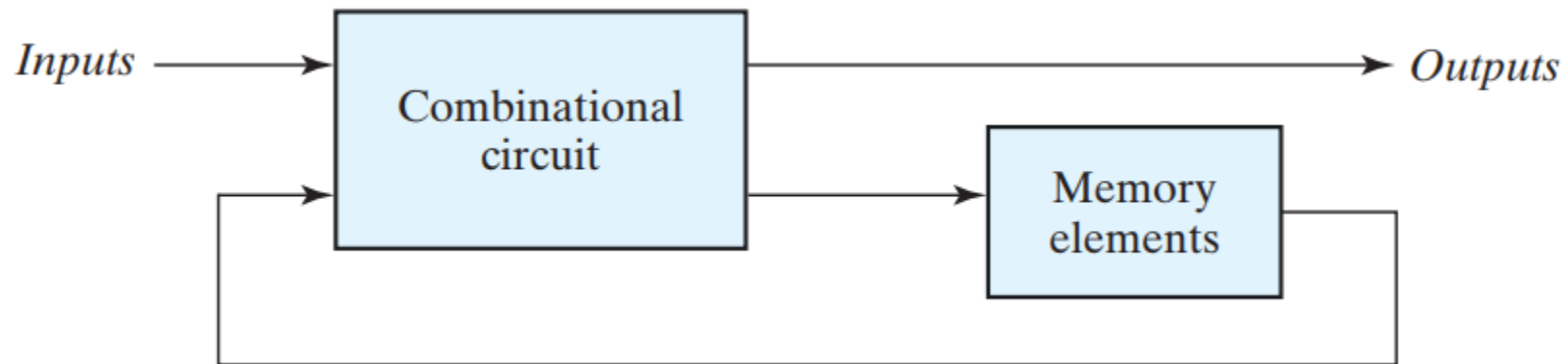


# Sequential logic circuits


# Sequential Circuit

- ❑ Output depends not only on current input but also on past input values
- ❑ Need some type of memory to remember the past input values



 
## Sequential Circuit

- ❑ It consists of a combinational circuit to which storage elements are connected to form a feedback path.
- ❑ The storage elements are devices capable of storing binary information.
- ❑ The binary information stored in these elements at any given time defines the *state* of the sequential circuit at that time.


 
## Clock Signal in Sequential Circuits


- ❑ The clock signal plays a crucial role in sequential circuits.
- ❑ A clock is a signal, which oscillates between logic level 0 and logic level 1, repeatedly.
- ❑ Square wave with constant frequency is the most common form of clock signal.


 
# Classification of Sequential Circuits

Based on the clock signal input, the sequential circuits are classified into two types

- Synchronous sequential circuit
- Asynchronous sequential circuit



## Synchronous Sequential Circuits

- ❑ In Synchronous sequential circuit, the output depends on present and previous states of the inputs at the clocked instances.
- ❑ The memory elements in these circuits will have clocks.
- ❑ These circuits are bit slower compared to asynchronous because they wait for the next clock pulse to arrive to perform the next operation

## Asynchronous Sequential Circuits

- ❑ The Sequential circuits which do not operate by clock signals are called “Asynchronous sequential circuits”.
- ❑ These circuits will change their state immediately when there is a change in the input signal .
- ❑ The Circuit behavior is determined by signals at any instant in time and the order in which input signals change


## Latches and Flip-flops

- ❑ Storage elements without a clock are called as latches.
- ❑ Storage elements which are controlled by a clock transition are called as flip-flops.



 
## S R Latch

- ❑ The *SR* latch is a circuit with two cross-coupled NOR gates or two cross-coupled NAND gates
- ❑ Two inputs labeled *S* for set and *R* for reset.
- ❑ The latch has two useful states.
- ❑ When output  $Q = 1$  and  $\bar{Q} = 0$ , the latch is said to be in the *set state*.
- ❑ When  $Q = 0$  and  $\bar{Q} = 1$ , it is in the *reset state*.
- ❑ Outputs  $Q$  and  $\bar{Q}$  are normally the complement of each other




## S R Latch

 


$S$	$R$	$Q$	$Q'$
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$ )
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$ )
1	1	0	0 (forbidden)

## S R Latch

 

S	R	Q
0	0	Q
0	1	0
1	0	1
1	1	Not allowed

## NAND & NOR gate

 


A	B	C
0	0	1
0	1	1
1	0	1
1	1	0



A	B	C
0	0	1
0	1	0
1	0	0
1	1	0


## S R Latch using NOR gate

 

$S$	$R$	$Q$	$Q'$
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$ )
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$ )
1	1	0	0 (forbidden)

- Under normal conditions, both inputs of the latch remain at 0 unless the state has to be changed.
- The application of a momentary 1 to the  $S$  input causes the latch to go to the set state.


## S R Latch using NAND gate

 

$S$	$R$	$Q$	$Q'$
1	0	1	0
1	1	1	0 (after $S = 1, R = 0$ )
0	1	0	1
1	1	0	1 (after $S = 0, R = 1$ )
0	0	1	1 (forbidden)



- ❑ It operates with both inputs normally at 1.
- ❑ The application of 0 to the  $S$  input causes output  $Q$  to go to 1, putting the latch in the set state.
 
## S R Latch using NAND gate and control input




$En$	$S$	$R$	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate

# J K Flip-flop

  



## J K Flip-flop

 


J	K	Q
0	0	Q
0	1	0
1	0	1
1	1	$\bar{Q}$

## Race Around Condition In JK Flip-flop


For J-K flip-flop, if  $J=K=1$ , and if  $\text{clk}=1$  for a long period of time, then Q output will toggle as long as CLK is high, which makes the output of the flip-flop unstable or uncertain. This problem is called race around condition in J-K flip-flop

- ❑ This can be avoided by ensuring that the clock input is at logic “1” only for a very short time.
- ❑ This led to the development of Master Slave JK flip flop.

# Master Slave JK flip flop

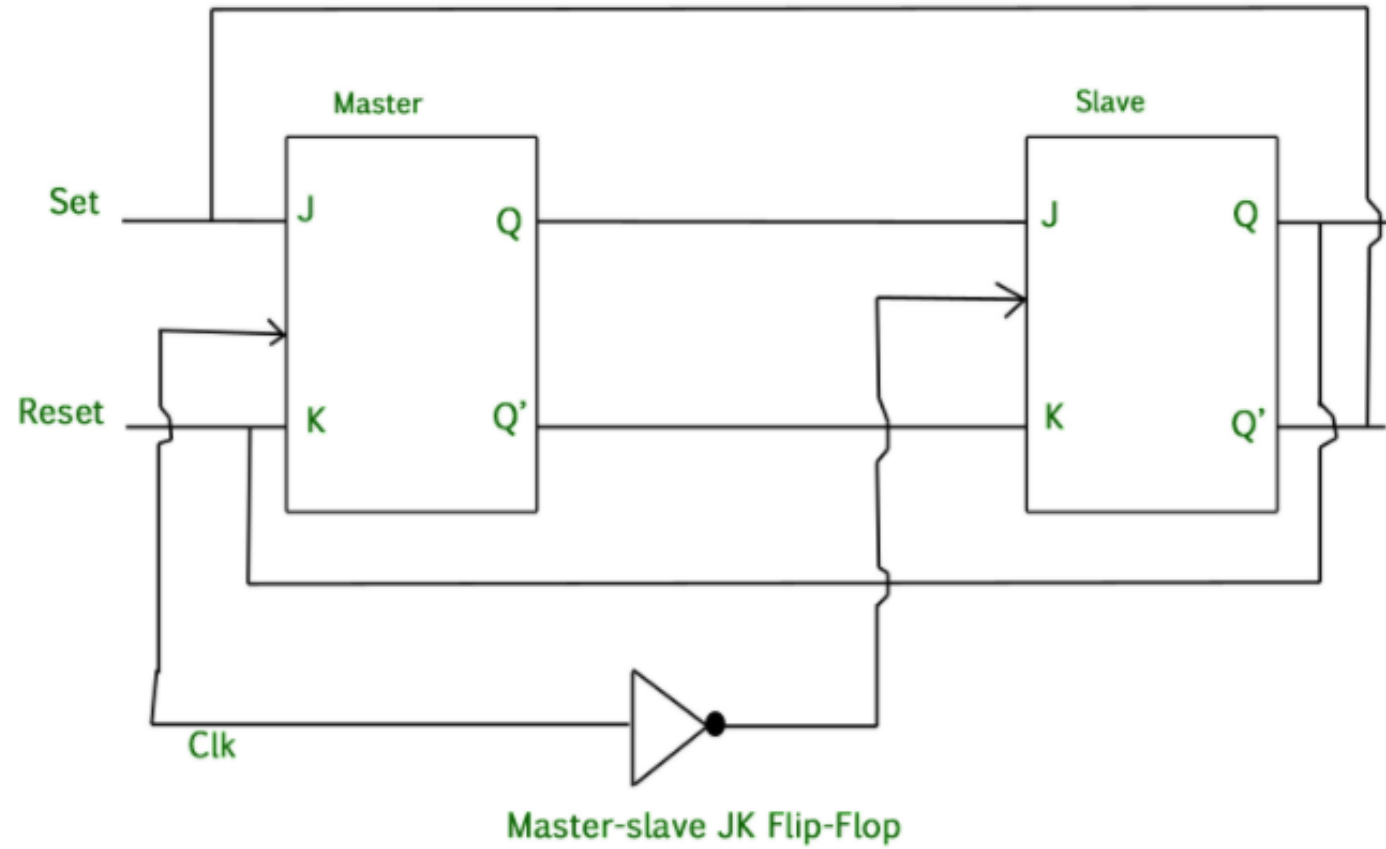

 
## S R Latch using NAND gate and control input




$En$	$S$	$R$	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate

# D-flip flop

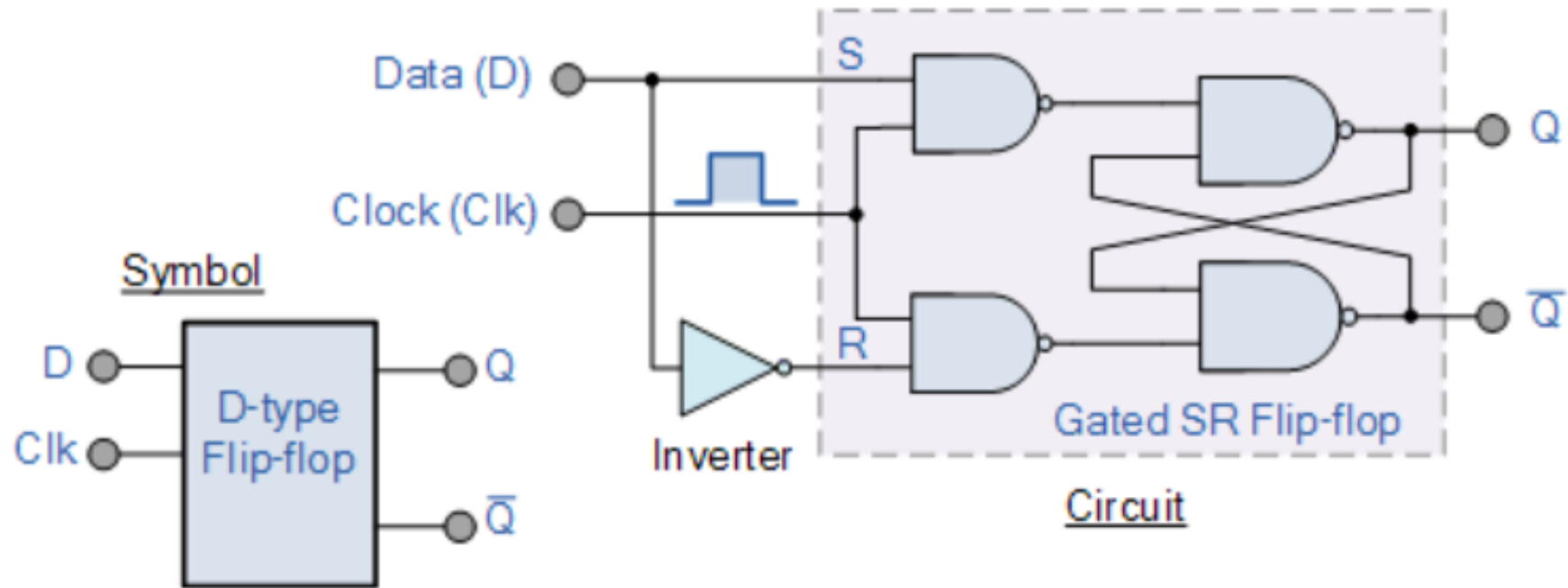


# D-flip flop

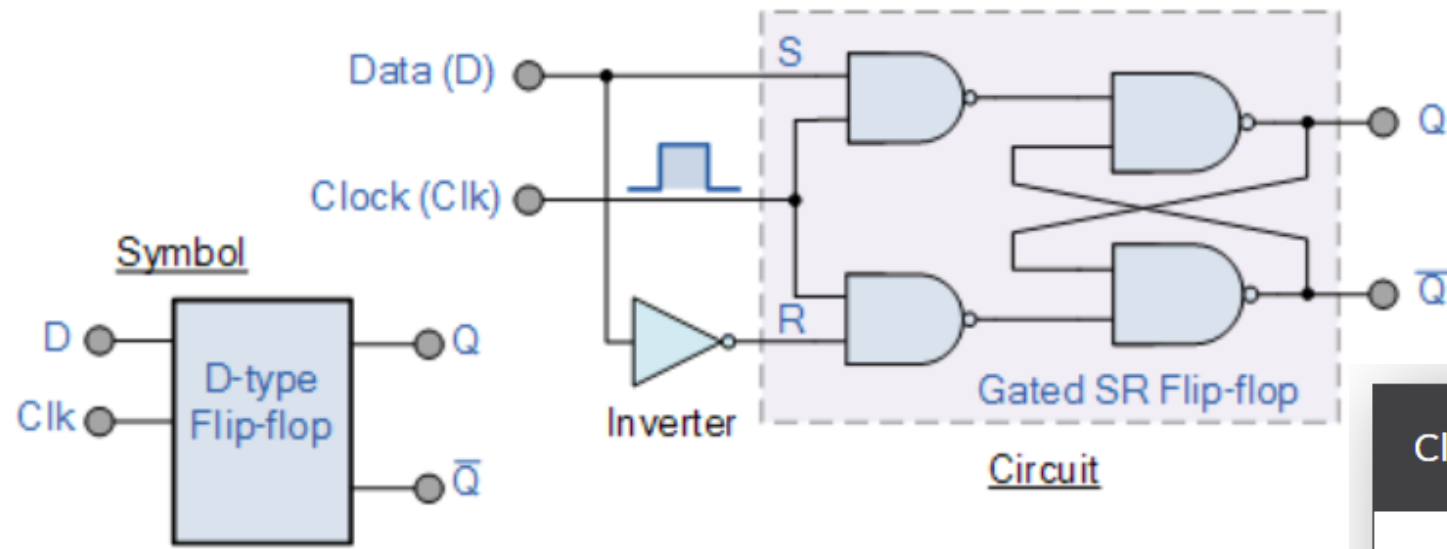


Clk	D	Q	$\bar{Q}$	Description
$\downarrow \gg 0$	X	Q	$\bar{Q}$	Memory no change
$\uparrow \gg 1$	0	0	1	Reset Q $\gg$ 0
$\uparrow \gg 1$	1	1	0	Set Q $\gg$ 1
 
## T-flip flop

T stands for the toggle. T flip-flop is modified version of JK flip-flop. JK inputs of JK flip-flop combine together to form a single input T. This flip-flop is called T flip-flop.



## T-flip flop

 



T	$Q_{\text{next}}$
0	Q
1	$\bar{Q}$

When  $T = 1$ , the output keeps changing  $Q = \bar{Q}$  upon each clock cycle.

 
When  $T = 0$ , the flip-flop hold its state  $Q = Q$ .





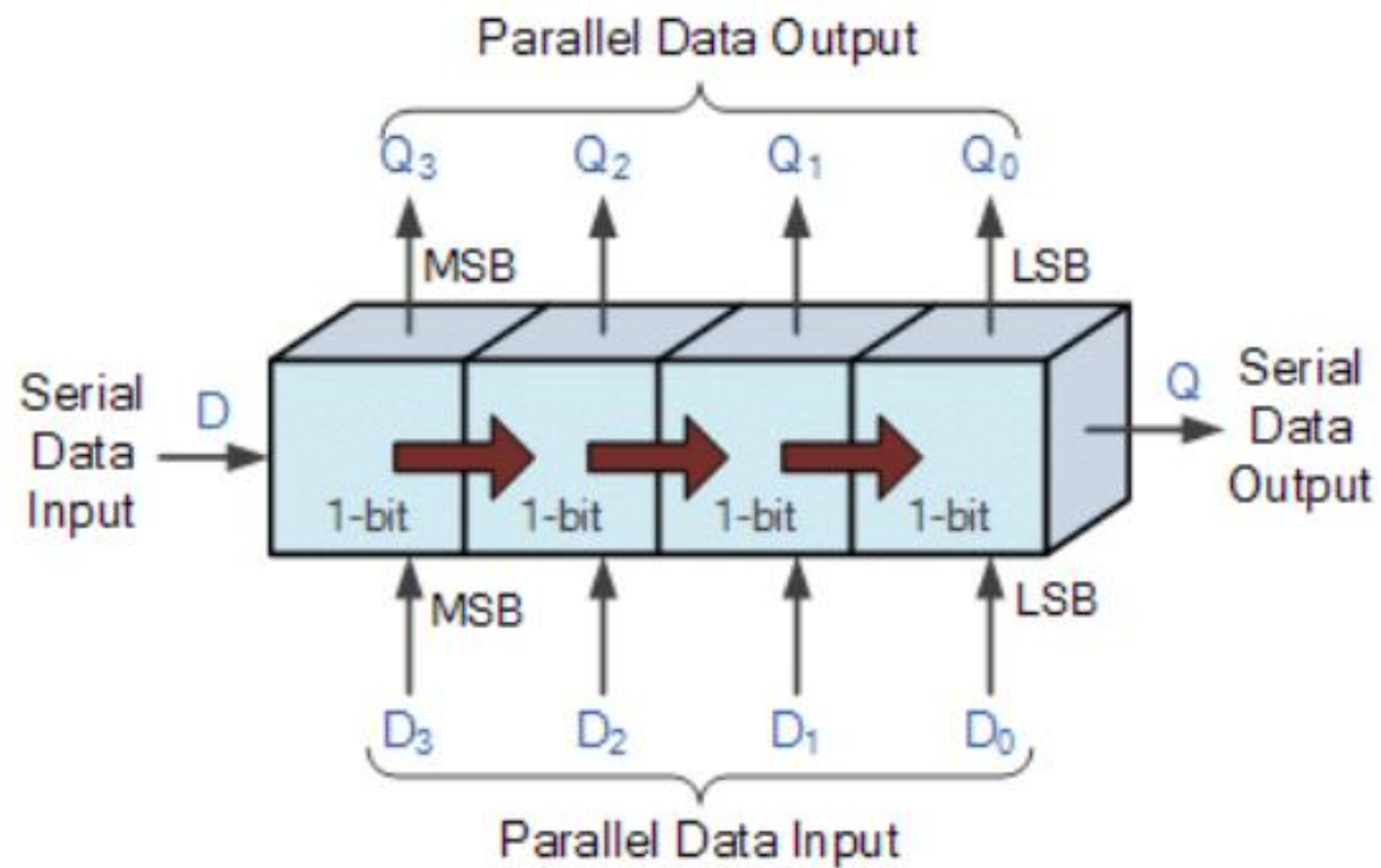

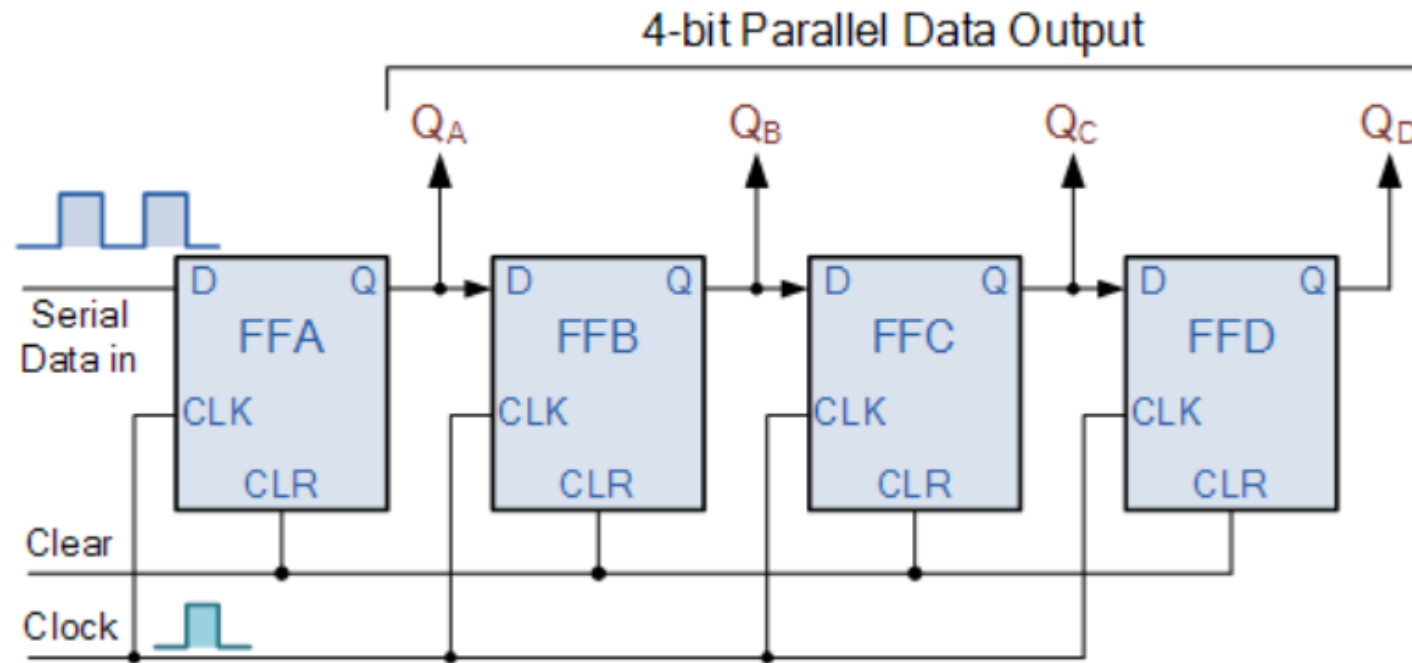
## 4 bit-serial-in Parallel-Out (SIPO) Shift Register




## 4 bit-serial in Parallel Out (SIPO) Shift Register

Clock Pulse No	QA	QB	QC	QD
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1
5	0	0	0	0

 

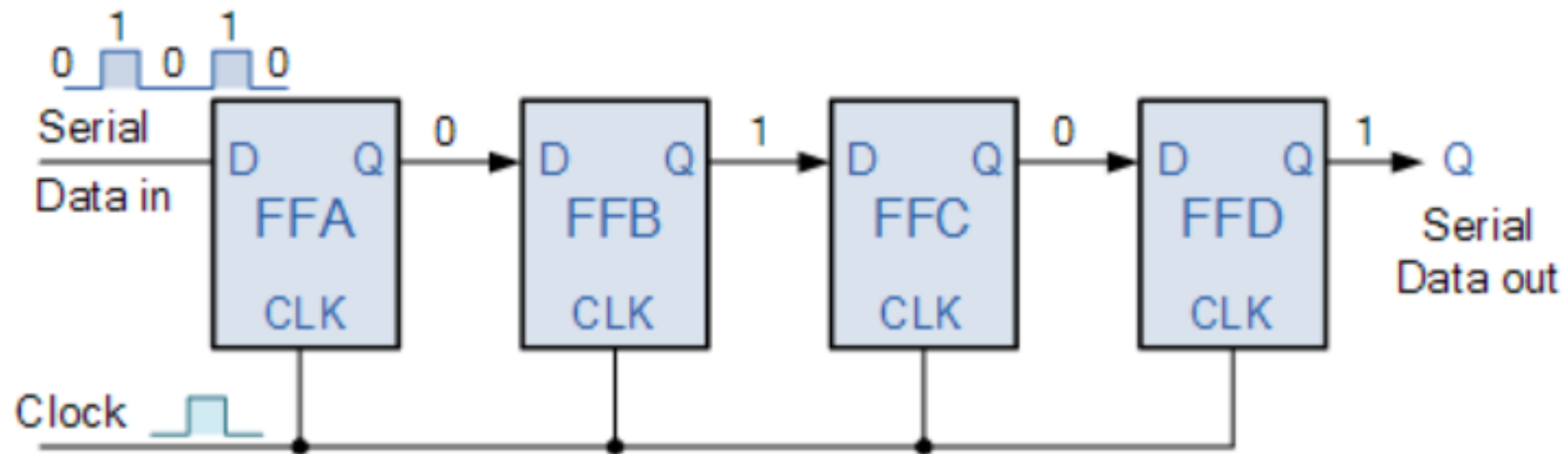
## 4-bit Serial-in to Serial-out Shift Register





This type of **Shift Register** also acts as a temporary storage device or it can act as a time delay device for the data
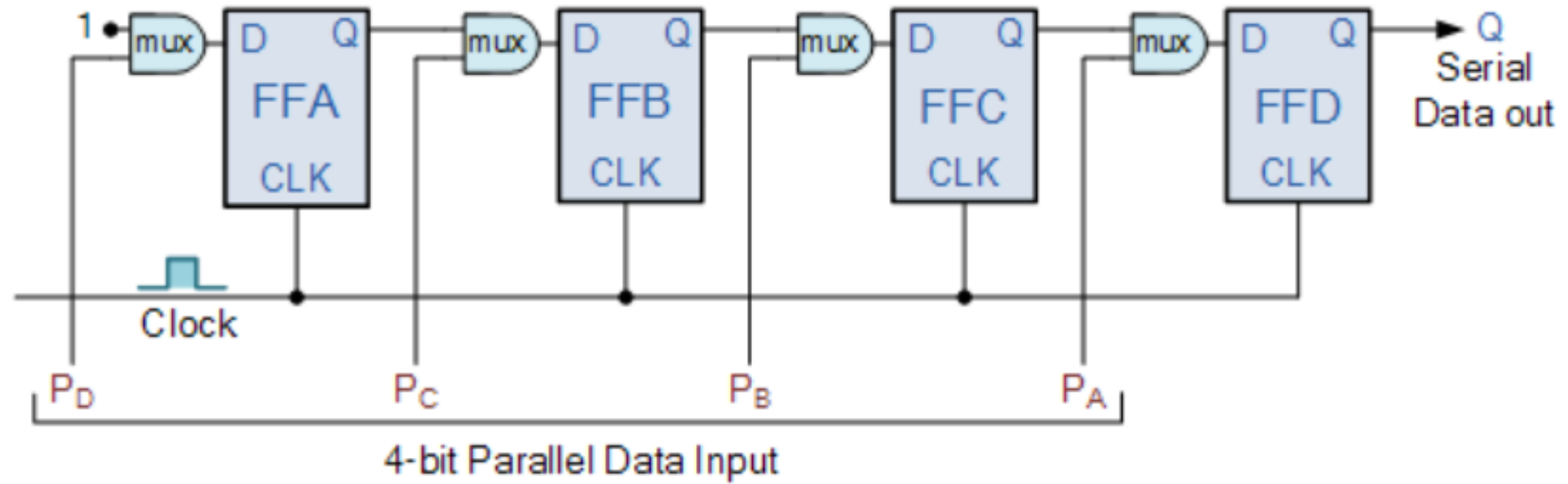
## 4-bit Parallel-in to Serial-out Shift Register


 
## 4-bit Parallel-in to Serial-out Shift Register



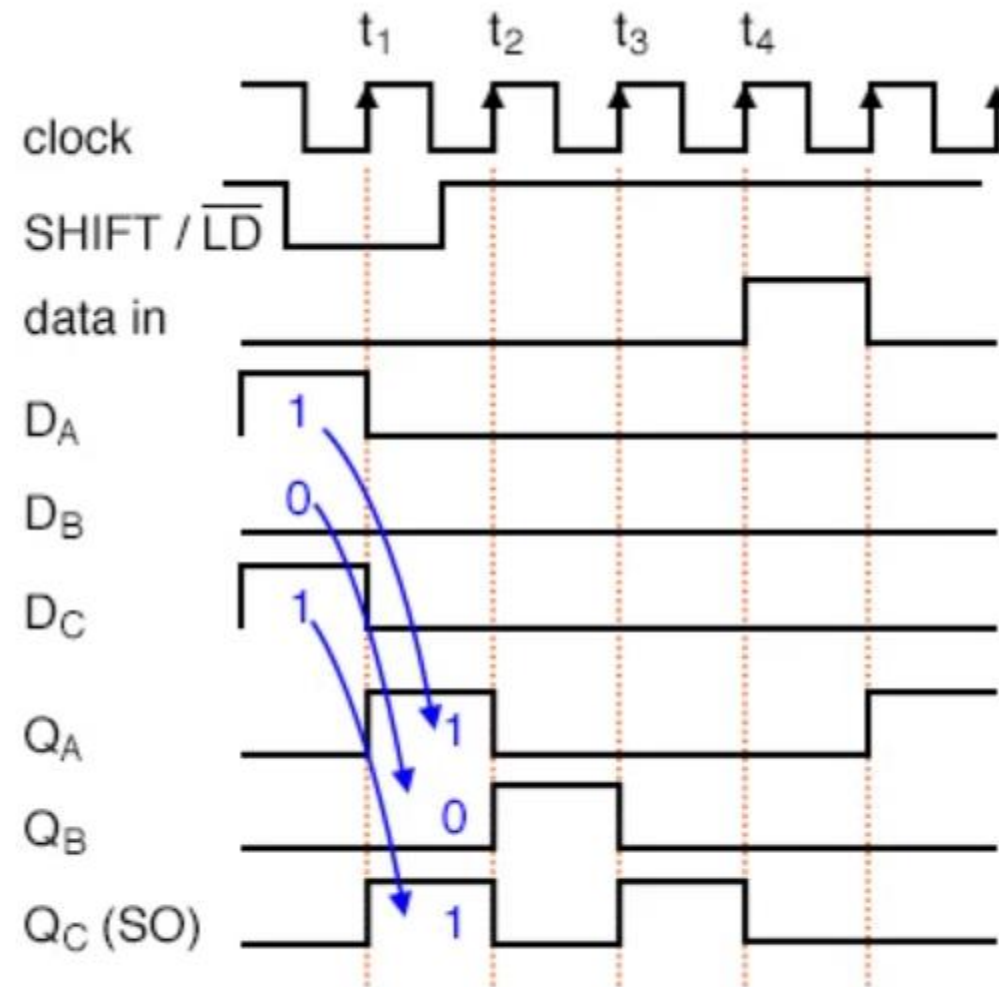

Parallel-in/ serial-out shift register load/ shift waveforms



## 4-bit Parallel-in to Parallel-out Shift Register

