


MODULE: 3

DC chopper

Chopper is a converter to convert fixed DC to Variable DC converter (simply DC to DC converter)

Step down (or step up) chopper

working:

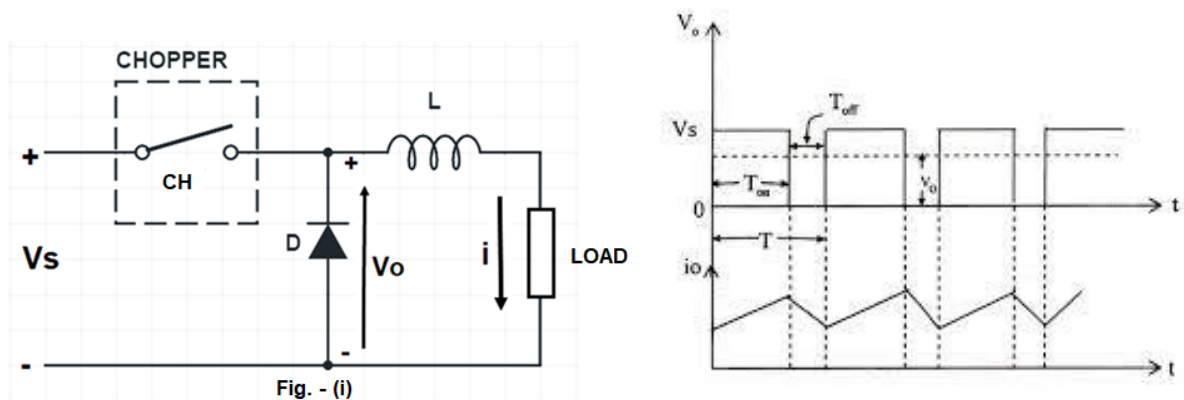

- Switch is ON, current flows through the inductor and load.
- Switch is OFF, the stored energy in the inductor discharged through the load and the freewheeling diode.
- Hence output voltage is less than the input voltage and it is called a step-down Chopper.
- Duty cycle, $\alpha = T_{on}/T$
- $T = T_{ON} + T_{OFF}$
- Output voltage $V_o = D.V_{in}$

Problems

1. A step-up chopper has input voltage of 220V and output voltage of 660V. If the total time period of thyristor-chopper is $300\mu s$, then compute its duty cycle (α) and turn ON time (T_{ON}).

Solution

$$V_{in} = 220V$$

$$V_o = 660V$$

$$T = 300\mu s$$

$$V_o = V_{in}/(1-\alpha)$$

$$660 = 220/(1-\alpha)$$

$$660 - 220 = 660\alpha$$

Solving $\alpha = 440/660 = 2/3$

$T_{ON} = \alpha T$

Solving $T_{ON} = 2/3 \times 300 = 200 \mu s$

2. A step-down chopper has input voltage of 440V and output voltage of 220V. If the total time period of thyristor-chopper is $300 \mu s$, then compute its duty cycle (D) and turn ON time (T_{ON})

Solution

$V_{in} = 440V$

$V_o = 220V$

$T = 300 \mu s$

$V_o = D V_{in}$

Duty ratio, $D = V_o/V_{in} = 220/440 = 0.5$



On time $T_{ON} = DT = 0.5 \times 300 \mu s = 150 \mu s$

Chopper control strategies

Output of dc voltage can be controlled by 2 methods

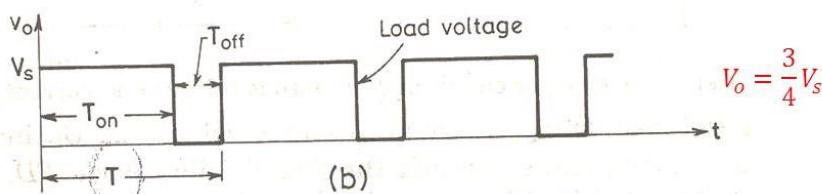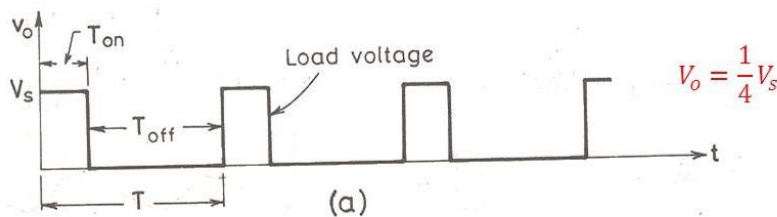(a) Constant frequency method


- In this method, ON time T_{ON} is varied keeping chopping frequency constant (ie, T is constant because $T = 1/f$).
- It is also called pulse width modulation scheme.
- Variation of T_{ON} means adjust the pulse width.




(b) Variable frequency method

- In this method, the chopping frequency is varied (ie, T is varied)
- It is also called frequency modulation scheme.

Keeping T_{on} constant

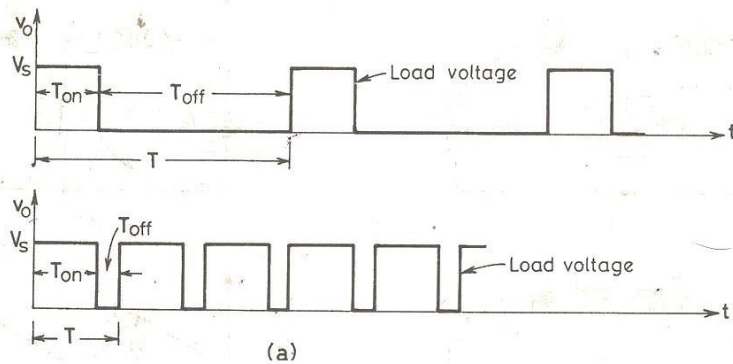

Keeping T_{off} constant

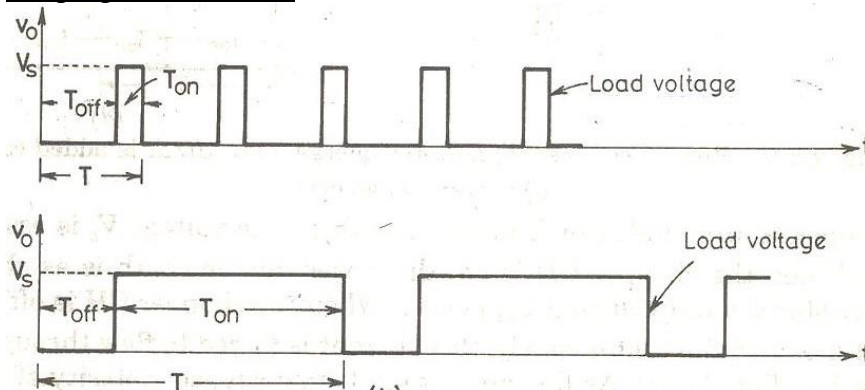


Types of choppers

Chopper is classified as follows,

1. Type A chopper or First quadrant chopper
2. Type B chopper or second quadrant chopper
3. Type C chopper or Two quadrant type A chopper
4. Type D chopper or Two quadrant type B chopper
5. Type E chopper or Fourth quadrant chopper

Type A chopper

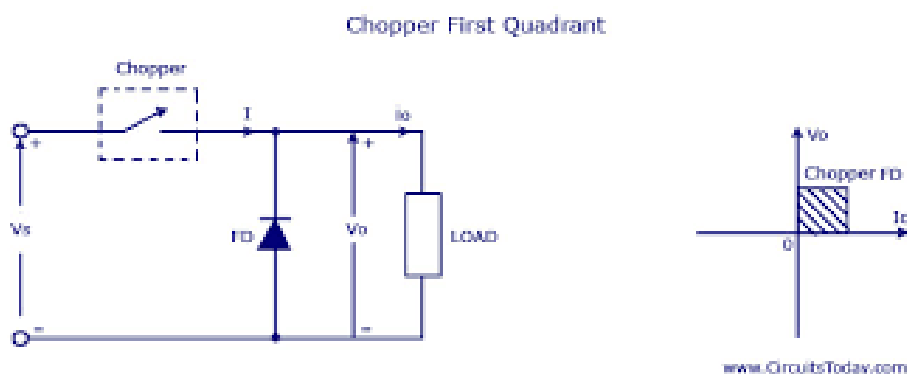

- Type A chopper works in the first quadrant.
- In this chopper, the voltage and current both are positive and flows in the same direction.

- When CH is on, $V_0 = V_s$ and current I_0 flows from source to load.
- When CH is on, $V_0 = 0$ but current I_0 flowing in the same direction through freewheeling diode.
- Power from source to load and the average output voltage is less than input DC voltage.

Type B chopper


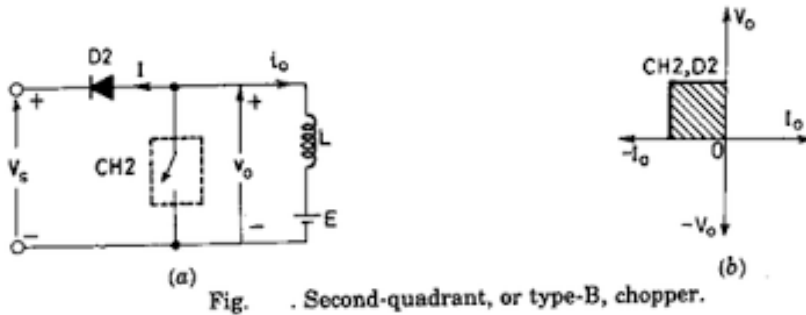


Fig. . Second-quadrant, or type-B, chopper.

- Type B chopper operates in second quadrant
- The load must always contain a dc source E .
- When the chopper is on, V_0 is zero but the load voltage E drives the current through the inductor L and the chopper. L stores energy
- Output current I_0 is negative.
- When the chopper is off, $V_0 = E + V_L$
- The load voltage will be more than the voltage V_s
- Since V_0 positive and the current I_0 negative. Power is negative
- Power flow will be from load to source.

Type C chopper

Chopper Two Quadrant

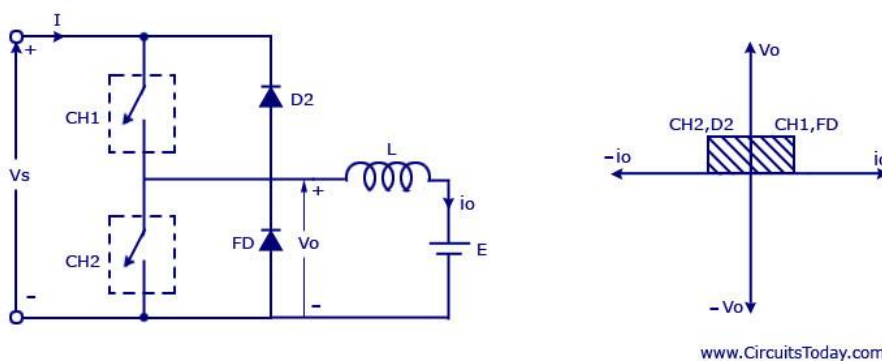


www.CircuitsToday.com

- It is the parallel combination of type A and type B chopper.
- It is a two-quadrant chopper.
- Type A operates in first quadrant. Power flows from source to load
- Type B operates in second quadrant. Power flows from load to source
- $V_s - CH_1 - FD - \text{Load (L\&E)}$ forms Type A chopper

- $V_s - D2 - CH2 - \text{Load (L\&E)}$ forms Type B chopper
- $V_o = 0$ when CH2 on and FD (freewheeling diode) conducts
- $V_o = V_s$ when CH1 on and D2 conducts
- $I_o = \text{positive}$ when CH1 on and FD conducts
- $I_o = \text{negative}$ when CH2 on and D2 conducts
- **Type D chopper**

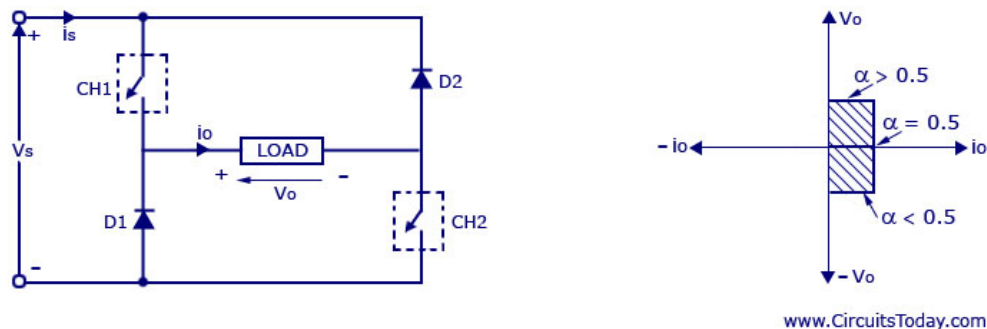
Two Quadrant Type B-chopper or D-chopper Circuit



- Two quadrant chopper.
- Operates in first and fourth quadrants.
- When CH1 and CH2 are on, current flows through $V_s - CH1 - \text{load} - CH2 - V_s$
- Output voltage $V_o = V_s$ is positive and I_o is positive
- When both choppers are off D1 & D2 conducts due to inductor in the load section. Output voltage is negative
- Current flows from load to source D1- V_s -D2-Load. I_o is positive

Type E chopper

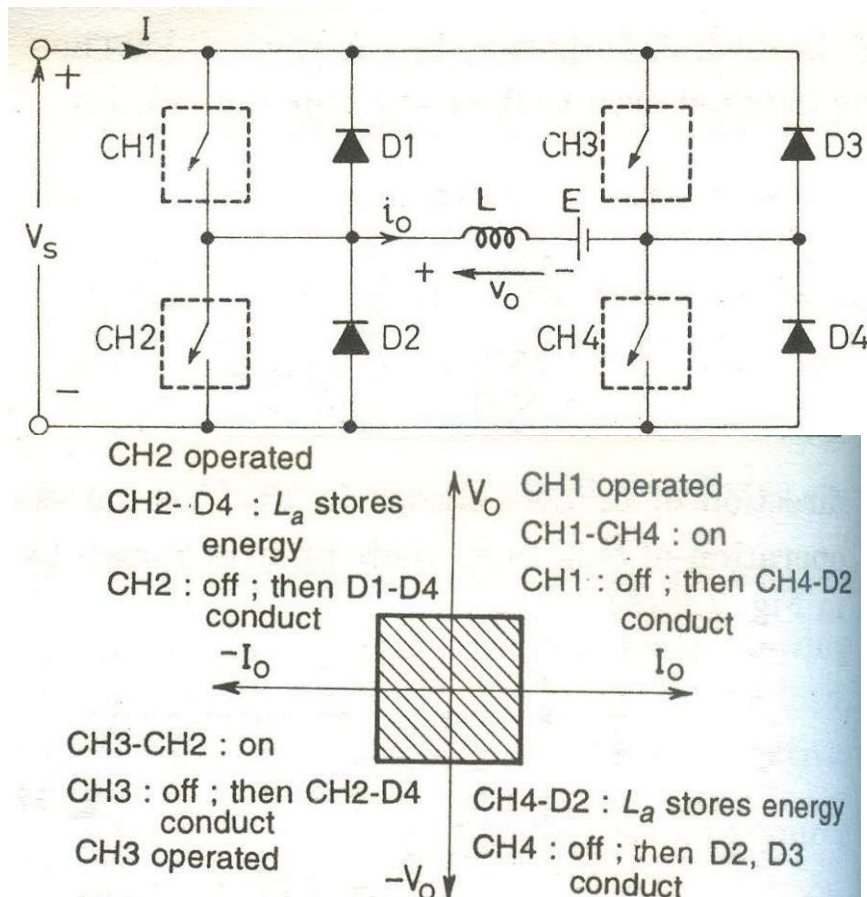
- The type E chopper is a four quadrant chopper.
- The type E chopper is parallel combination of two type C chopper.
- chopper CH1, chopper CH2, diode D1 and diode D2 makes one type C chopper
- chopper CH3, chopper CH4, diode D3 and diode D4 forms the other type C chopper.



Applications of chopper


- Switched mode power supplies, including DC to DC converters.
- Speed controllers for DC motors
- Driving brushless DC torque motors or stepper motors in actuators
- Class D electronic amplifiers
- Switched capacitor filters
- Variable-frequency drives
- D.C. voltage boosting
- Battery-operated electric cars
- Battery chargers
- Railway traction
- Lighting and lamp control

Buck converter

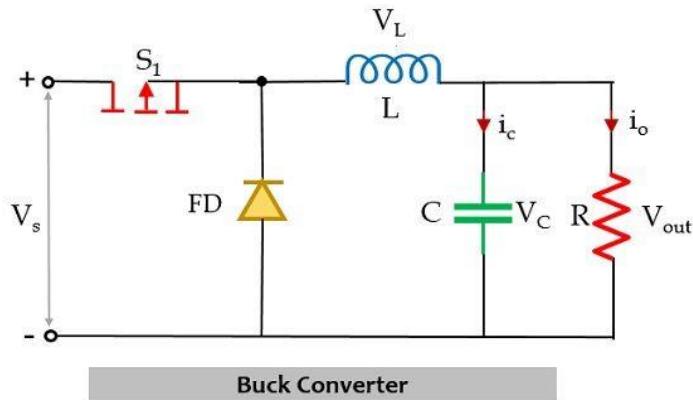

- It is a dc to dc converter.
- o/p voltage is less than input voltage.
- Power mosfet or IGBT is used as the controller switch.
- 2 modes of operation.
 - **Mode:1(switch S1 is closed)**
 - ✓ Current flows through voltage source, s1, inductor L and load R
 - ✓ Power delivered to load
 - ✓ Inductor stores energy
 - ✓ This period is called ON time (T_{on}) of buck converter
 - **Mode :2 (switch S1 is open)**
 - ✓ Energy stored in L delivered to load
 - ✓ Continuous current is obtained through freewheeling diode.
 - ✓ Capacitor smoothens the o/p current.
 - ✓ This period is called Off (T_{off}) time.

Boost Converter

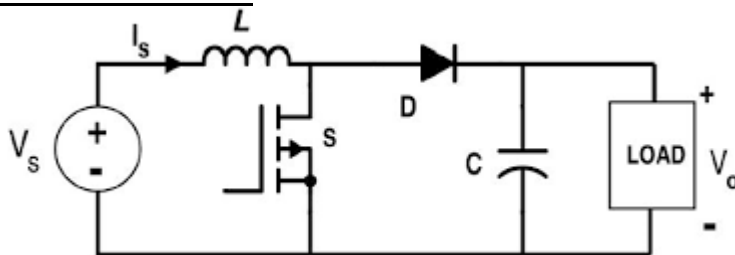

- It is a dc to dc converter
- o/p voltage is less than input voltage.
- V_s is connected in series with inductor
- 2 modes of operation.
 - **Mode 1 (S is closed)**
 - Source is directly connected to inductor L
 - L offer zero resistance to current
 - Current flows through V_s - L-S- V_s
 - Inductor stores energy
 - This period of operation is called T_{on} time
 - **Mode 2 (S is open)**

- Diode forward biased
- Current flows through V_s -L-D-load- V_s
- Input voltage V_s and energy stored in L obtained across load as o/p voltage

Comparison of Buck and Boost converter

Sl.No	Buck converter	Boost converter
1	o/p voltage is less than i/p voltage	o/p voltage is higher than i/p voltage
2	Large filters are required	Small filters are required
3	Poor power factor correction	High power factor correction
4	Also called step down converter	Also called step up converter
5	The input current is discontinuous in nature	the input current is continuous in nature
6	Not suited for PV cells	Suited for PV cells
7	Used in self-regulating power supplies, advanced telecommunication and data communication systems	They are used in regulated power supplies, regenerative braking of DC motor and portable device applications

Cycloconverters

- Cycloconverters convert AC power of fixed frequency to AC power of variable frequency.
- It is an AC to AC converter without using dc link.

Types of cycloconverter


I. Based on output frequency

- Step up cycloconverter (o/p frequency > i/p frequency)
- Step down cycloconverter(o/p frequency < i/p frequency)

II. Based on no.of phases

- 1ϕ to 1ϕ
- 3ϕ to 3ϕ
- 3ϕ to 1ϕ

Single phase step up cycloconverter

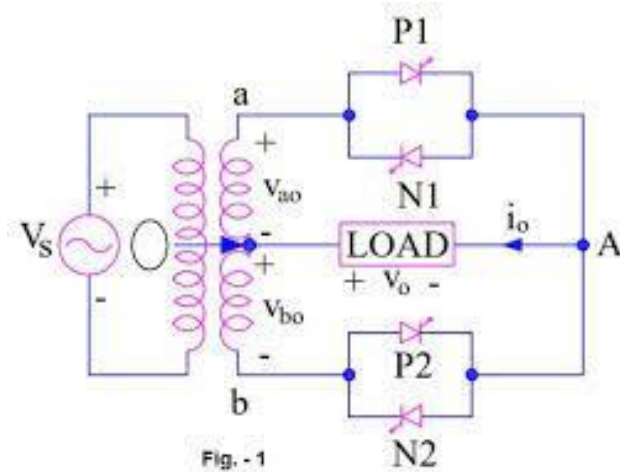

- During the positive half cycle, positive group thyristors P1 & N2 are forward biased for $\omega t = 0$ to $\omega t = \pi$.
- SCR P1 is fired to turn it.
- Load voltage is positive with terminal A positive and O negative.
- At $\omega t = \omega t_1$, P1 is force commutated and the forward biased thyristor N2 is fired to turn it ON.
- During the period N2 conducts, the load voltage is negative because O is positive & this time.
- At $\omega t = \omega t_2$, N2 is force commutated and P1 is turned ON.
- The load voltage is now positive.
- At $\omega t = \pi$, terminal “b” is positive with respect to terminal “a”; both SCRs P2 & N1 are therefore forward biased from $\omega t = \pi$ to $\omega t = 2\pi$.
- When P2 is turned on, the load voltage is positive
- To make the load voltage negative P2 is force commutated and N1 is triggered
- This process is repeated in the negative half cycle
- The frequency of output wave form is greater than input voltage and it is determined by proper switching of SCRs

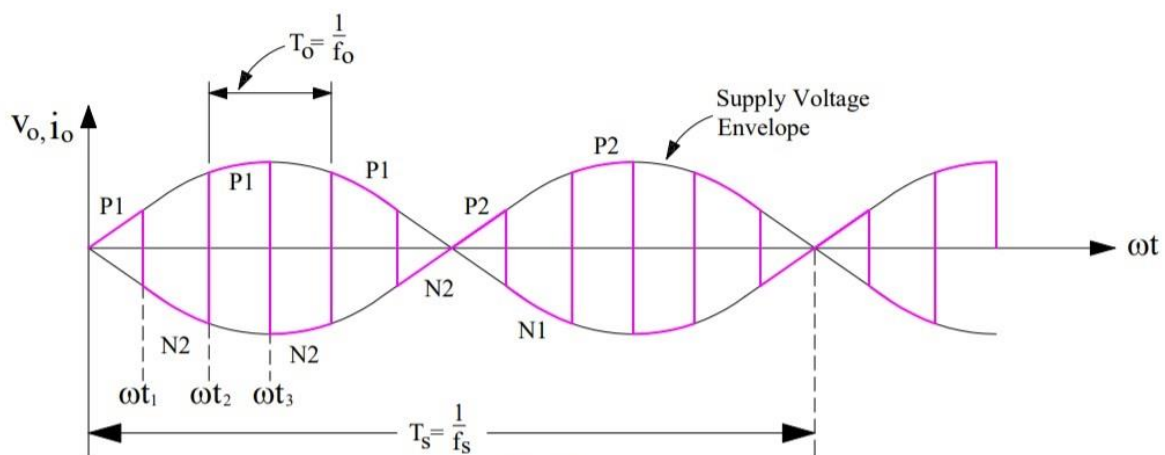


Fig. - 2

